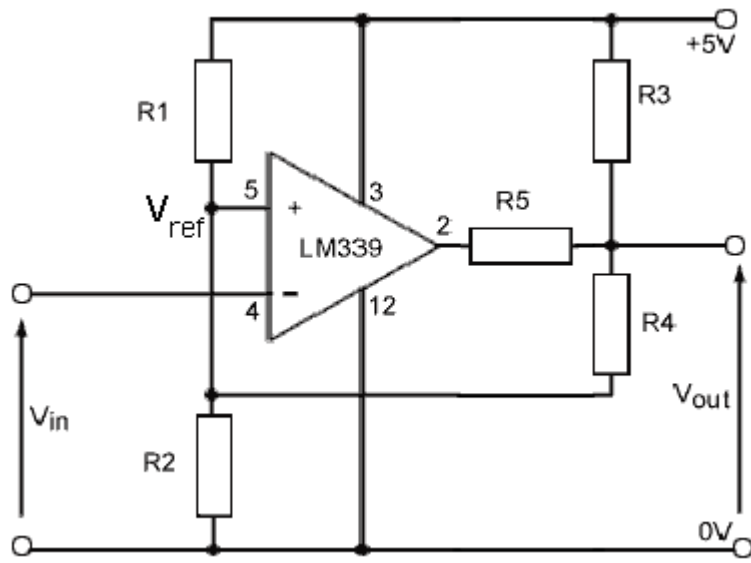


Open-Drain Schmitt Trigger with Programmable Low Level



Normalized High Output Voltage

Circuit equations for high output voltage case

Given

$$V_H \cdot \left(\frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{V_{TH\uparrow}}{R_4} - \frac{1}{R_3} = 0 \quad V_{TH\uparrow} \cdot \left(1 + \frac{1}{R_2} + \frac{1}{R_4} \right) - 1 - \frac{V_H}{R_4} = 0$$

$$\text{eq1} := \text{Find}(R_4, V_{TH\uparrow}) \rightarrow \left(\begin{array}{c} \frac{R_2 \cdot V_H - R_2 \cdot R_3 - R_2 + R_3 \cdot V_H + R_2 \cdot R_3 \cdot V_H}{R_2 - V_H - R_2 \cdot V_H + 1} \\ \frac{R_2 + R_2 \cdot R_3 - R_2 \cdot V_H}{R_3 + R_2 \cdot R_3} \end{array} \right)$$

Circuit equations for low output voltage case

Given

$$V_L \cdot \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_{TH\downarrow}}{R_4} - \frac{1}{R_3} - \frac{V_{OL}}{R_5} = 0 \quad V_{TH\downarrow} \cdot \left(1 + \frac{1}{R_2} + \frac{1}{R_4} \right) - 1 - \frac{V_L}{R_4} = 0$$

$$\text{eq2} := \text{Find}(R_5, V_{TH\downarrow}) \rightarrow \left(\begin{array}{c} \frac{R_2 \cdot R_3 \cdot V_L + R_3 \cdot R_4 \cdot V_L - R_2 \cdot R_3 \cdot V_{OL} - R_3 \cdot R_4 \cdot V_{OL} + R_2 \cdot R_3 \cdot R_4 \cdot V_L - R_2 \cdot R_3 \cdot R_4 \cdot V_{OL}}{R_2 \cdot V_L - R_4 - R_2 \cdot R_3 - R_2 \cdot R_4 - R_2 + R_3 \cdot V_L + R_4 \cdot V_L + R_2 \cdot R_3 \cdot V_L + R_2 \cdot R_4 \cdot V_L} \\ \frac{R_2 \cdot R_4 + R_2 \cdot V_L}{R_2 + R_4 + R_2 \cdot R_4} \end{array} \right)$$

Solve For Normalized Resistance Values

Given

$$R_4 = \frac{R_2 \cdot V_H - R_2 \cdot R_3 - R_2 + R_3 \cdot V_H + R_2 \cdot R_3 \cdot V_H}{R_2 - V_H - R_2 \cdot V_H + 1} \quad V_{TH\downarrow} = \frac{R_2 \cdot R_4 + R_2 \cdot V_L}{R_2 + R_4 + R_2 \cdot R_4}$$

$$V_{TH\uparrow} = \frac{R_2 + R_2 \cdot R_3 - R_2 \cdot V_H}{R_3 + R_2 \cdot R_3}$$

$$\text{eq1} := \text{Find}(R_2, R_3, R_4) \rightarrow \left(\begin{array}{c} -1 \\ V_H - 1 \\ V_{TH\downarrow} - V_L \end{array} \right) \left(\begin{array}{c} \frac{V_H \cdot V_{TH\downarrow} - V_L \cdot V_{TH\uparrow}}{V_H - V_L - V_{TH\uparrow} + V_{TH\downarrow} - V_H \cdot V_{TH\downarrow} + V_L \cdot V_{TH\uparrow}} \\ \frac{V_H^2 \cdot V_{TH\downarrow} - V_H \cdot V_{TH\downarrow} + V_L \cdot V_{TH\uparrow} - V_H \cdot V_L \cdot V_{TH\uparrow}}{V_{TH\uparrow}^2 - V_H \cdot V_{TH\uparrow} + V_H \cdot V_{TH\downarrow} - V_{TH\uparrow} \cdot V_{TH\downarrow}} \\ \frac{V_H \cdot V_{TH\downarrow} - V_L \cdot V_{TH\uparrow}}{V_{TH\uparrow} - V_{TH\downarrow}} \end{array} \right)$$

extraneous solution

desired solution

$$R_2(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) := \frac{V_H \cdot V_{TH\downarrow} - V_L \cdot V_{TH\uparrow}}{V_H - V_L - V_{TH\uparrow} + V_{TH\downarrow} - V_H \cdot V_{TH\downarrow} + V_L \cdot V_{TH\uparrow}}$$

$$R_3(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) := \frac{V_H^2 \cdot V_{TH\downarrow} - V_H \cdot V_{TH\downarrow} + V_L \cdot V_{TH\uparrow} - V_H \cdot V_L \cdot V_{TH\uparrow}}{V_{TH\uparrow}^2 - V_H \cdot V_{TH\uparrow} + V_H \cdot V_{TH\downarrow} - V_{TH\uparrow} \cdot V_{TH\downarrow}}$$

$$R_4(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) := \frac{V_H \cdot V_{TH\downarrow} - V_L \cdot V_{TH\uparrow}}{V_{TH\uparrow} - V_{TH\downarrow}}$$

Solving for R5 in terms of specification parameters did not prove workable. The expression was too large to display. I will instead compute R5 using a formula expressed in terms of other resistance values.

Explicit Formula for R5

$$R_5(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) := \begin{cases} R_2 \leftarrow R_2(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) \\ R_3 \leftarrow R_3(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) \\ R_4 \leftarrow R_4(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) \\ \frac{R_2 \cdot R_3 \cdot V_L + R_3 \cdot R_4 \cdot V_L - R_2 \cdot R_3 \cdot V_{OL} - R_3 \cdot R_4 \cdot V_{OL} + R_2 \cdot R_3 \cdot R_4 \cdot V_L - R_2 \cdot R_3 \cdot R_4 \cdot V_{OL}}{R_2 \cdot V_L - R_4 - R_2 \cdot R_3 - R_2 \cdot R_4 - R_2 + R_3 \cdot V_L + R_4 \cdot V_L + R_2 \cdot R_3 \cdot V_L + R_2 \cdot R_4 \cdot V_L} \end{cases}$$

Worked Example

$$V_{CC} := 10 \quad V_H := \frac{8}{V_{CC}} = 0.8 \quad V_{TH\downarrow} := \frac{4 - 0.4}{V_{CC}} \quad V_{TH\uparrow} := \frac{4 + 0.4}{V_{CC}} \quad V_L := \frac{2}{V_{CC}} \quad V_{OL} := \frac{0}{V_{CC}}$$

$$r_1 := 1$$

$$r_2 := R_2(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) = 0.625000$$

$$r_3 := R_3(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) = 1.388889$$

$$r_4 := R_4(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) = 2.500000$$

$$r_5 := R_5(V_H, V_{TH\downarrow}, V_{TH\uparrow}, V_L, V_{OL}) = 0.3125$$

Unnormalized Values

$$R_1 := 10\text{K}\Omega$$

$$R_2 := r_2 \cdot R_1 = 6.25 \cdot \text{k}\Omega$$

$$R_3 := r_3 \cdot R_1 = 13.88889 \cdot \text{K}\Omega$$


$$R_4 := r_4 \cdot R_1 = 25.000000 \cdot \text{k}\Omega$$

$$R_5 := r_5 \cdot R_1 = 3.125 \cdot \text{K}\Omega$$

$$V_H := V_H \cdot V_{CC} = 8$$

LTSpice Simulation of Real Comparator

LTSpice Circuit

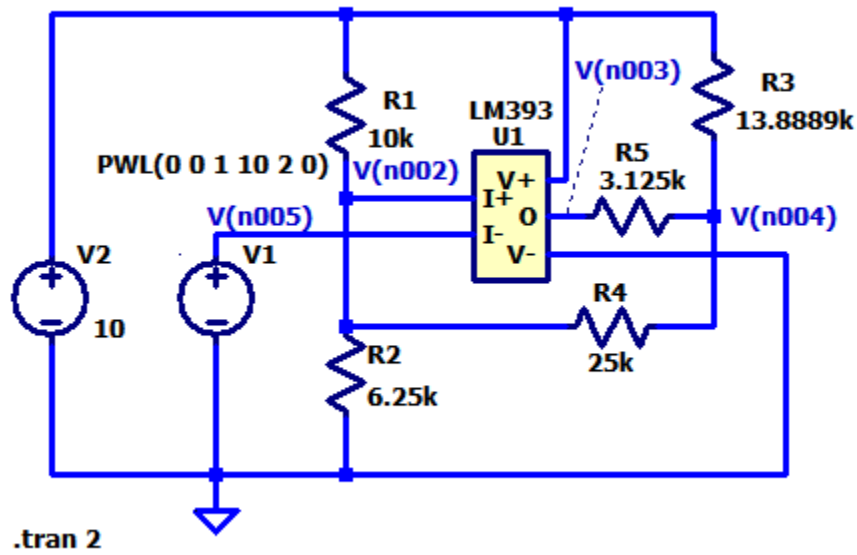

LTSpice Simulation

