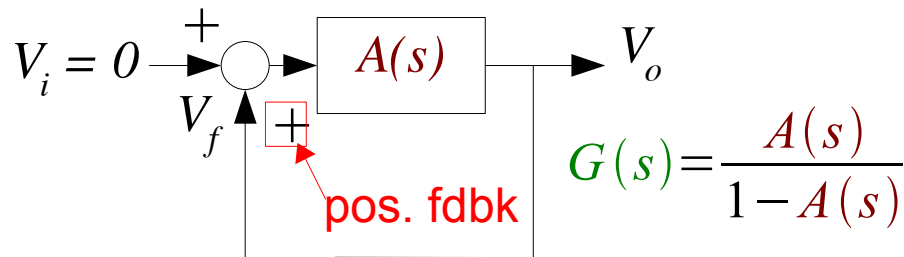


Colpitts Oscillator

- Basic positive feedback oscillator
- The Colpitts LC Oscillator circuit
- Open-loop analysis
- Closed-loop analysis
- Root locus
- Stability limit
- Colpitts design

Basic Positive Feedback Oscillator

closed-loop oscillator




$$V_o = A(s)(V_i + V_f) = A(s)(0 + V_o) \Rightarrow$$

$$V_o(1 - A(s)) = 0$$

Since: $V_o \neq 0 \Rightarrow 1 - A(s) = 0 \Rightarrow A(s) = 1 \Rightarrow \boxed{D(s) - K N(s) = 0}$


Condition for oscillation at $s = j\omega_0$: $\boxed{A(s) = 1 e^{j\pm 2k\pi}}$ ← Barkhausen criterion
for $k = 0, 1, 2 \dots$

open-loop: determine loop-gain

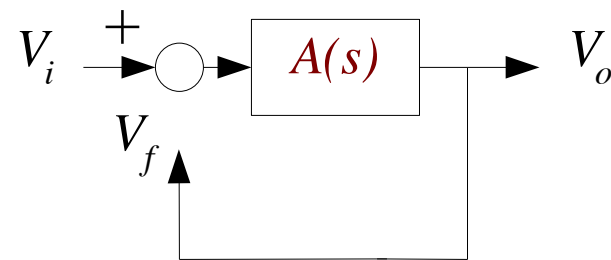


$$\frac{V_f}{V_i} = \frac{V_o}{V_i} = A(s) = \frac{K N(s)}{D(s)}$$

Colpitts Oscillator Basic Schematic

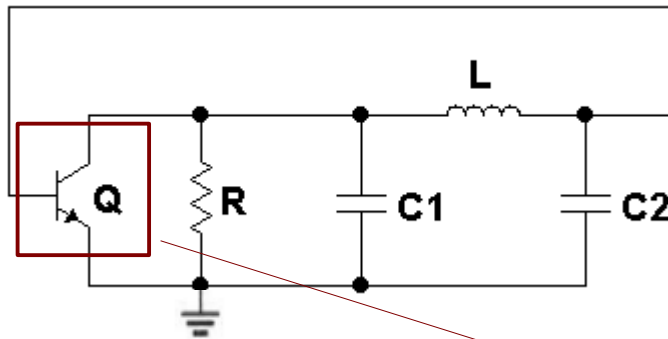


Emphasizing feedback

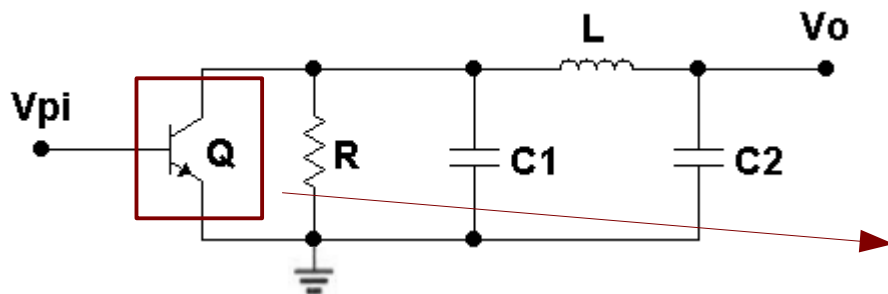


Emphasizing loop gain $\Gamma_F A(s)$

Assumptions:

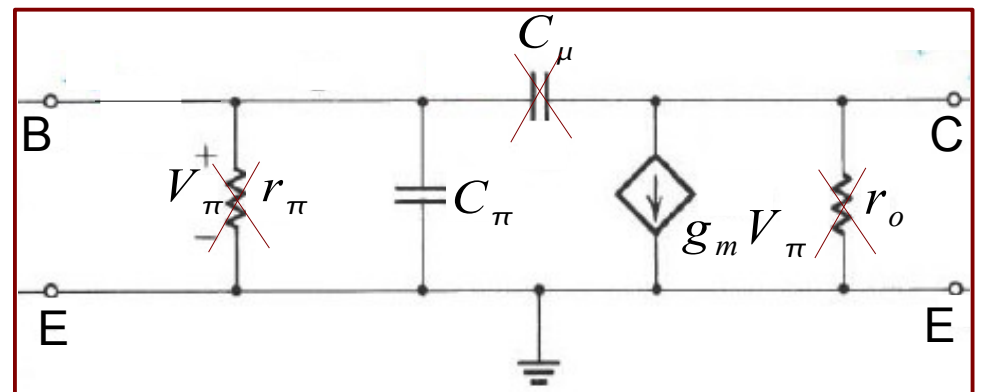1. r_π large (compared to $1/\omega C_2$).
2. C_μ negligible (compared to C_1, C_2)
3. C_π part of C_2 (in closed loop)
4. R represents total resistance in collector circuit, i.e. $R \parallel r_o \approx R$



Loop-Gain Analysis

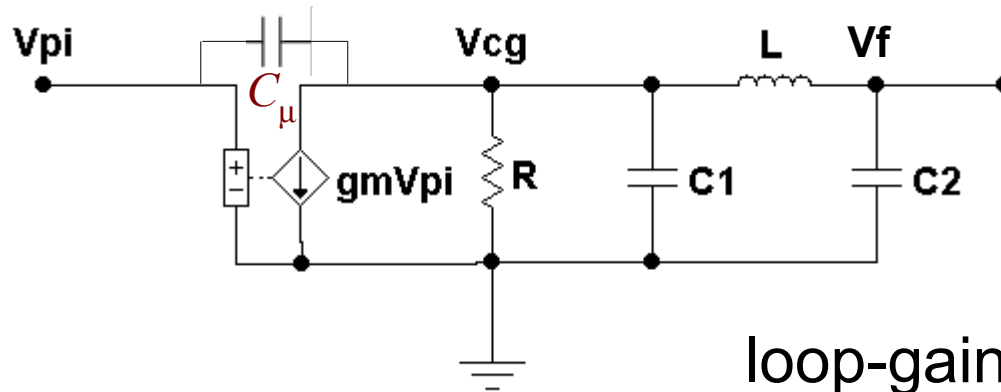

loop-gain: $A(s) = \frac{V_f}{V_\pi}$

Node equation at v_{cg} :

$$(g_m - sC_\mu)V_\pi + \frac{V_{cg}}{R} + s(C_1 + C_\mu)V_{cg} + \frac{(V_{cg} - V_f)}{sL} = 0$$

Note that

$$V_f = V_f(s)$$

$$V_{cg} = V_{cg}(s)$$

$$V_\pi = V_\pi(s)$$

at v_f :

$$\frac{(V_f - V_{cg})}{sL} + sC_2V_f = 0$$

Open Loop Analysis - cont.

Rearranging the two equations:

$$\left(sC_1 + \frac{1}{sL} + \frac{1}{R} \right) V_{cg} - \frac{1}{sL} V_f = (sC_\mu - g_m) V_\pi$$

$$-\frac{1}{sL} V_{cg} + \left(sC_2 + \frac{1}{sL} \right) V_f = 0$$

Further rearrangement:

$$\left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) V_{cg} - \frac{1}{sL} V_f = (sC_\mu - g_m) V_\pi$$

$$-\frac{1}{sL} V_{cg} + \left(\frac{s^2 LC_2 + 1}{sL} \right) V_f = 0$$

from previous slide

$$(g_m - sC_\mu) V_\pi + \frac{V_{cg}}{R} + s(C_1 + C_\mu) V_{cg} + \frac{(V_{cg} - V_f)}{sL} = 0$$

$$\frac{(V_f - V_{cg})}{sL} + sC_2 V_f = 0$$



Open Loop Analysis - cont.

from previous slide

$$\left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right) V_{cg} - \frac{1}{sL} V_f = (sC_\mu - g_m) V_\pi \quad (1)$$

Prepare to add the two equations:

$$-\frac{1}{sL} V_{cg} + \left(\frac{s^2 LC_2 + 1}{sL}\right) V_f = 0 \quad (2)$$

$$\frac{1}{sL} \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right) V_{cg} - \left(\frac{1}{sL}\right)^2 V_f = \frac{sC_\mu - g_m}{sL} V_\pi$$

Eq(1) * $\frac{1}{sL}$

$$-\frac{1}{sL} \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right) V_{cg} + \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right) \left(\frac{s^2 LC_2 + 1}{sL}\right) V_f = 0$$

Eq(2) * $\left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right)$

Adding (V_{cg} terms cancel):

$$\left(-\left(\frac{1}{sL}\right)^2 + \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right) \left(\frac{s^2 LC_2 + 1}{sL}\right)\right) V_f = \frac{sC_\mu - g_m}{sL} V_\pi$$



Open Loop Analysis – cont.

From previous slide

$$\left(-\left(\frac{1}{sL}\right)^2 + \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R}\right) \left(\frac{s^2 LC_2 + 1}{sL}\right) \right) V_f = \frac{C_\mu - g_m}{sL} V_\pi$$

Multiply by $(sL)^2$:

$$\left(-1 + \left(s^2 LC_1 + 1 + \frac{sL}{R}\right) (s^2 LC_2 + 1) \right) V_f = (sC_\mu - g_m) sL V_\pi$$

Expand and collect terms according to s^n :

$$\left(-1 + s^4 C_1 C_2 L^2 + s^2 (LC_1 + LC_2) + s^3 \frac{L^2 C_2}{R} + s \frac{L}{R} + 1 \right) V_f = (sC_\mu - g_m) sL V_\pi$$

Open Loop Analysis - cont.

From previous slide

$$\left(-\cancel{1} + s^4 C_1 C_2 L^2 + s^2 (L C_1 + L C_2) + \frac{s^3 L^2 C_2}{R} + \frac{s L}{R} + \cancel{1} \right) V_f = (s C_\mu - g_m) s L V_\pi$$

Canceling $(-1$ by $1)$ and dividing by sL :

$$\left(s^3 C_1 C_2 L + s (C_1 + C_2) + \frac{s^2 L C_2}{R} + \frac{1}{R} \right) V_f = (s C_\mu - g_m) V_\pi$$

Multiply by R :

$$\left(s^3 R C_1 C_2 L + s R (C_1 + C_2) + s^2 L C_2 + 1 \right) V_f = (s C_\mu - g_m) R V_\pi$$

Open Loop Analysis - cont.

From previous slide

$$\left(s^3 RC_1 C_2 L + s R(C_1 + C_2) + s^2 LC_2 + 1 \right) V_f = (s C_\mu - g_m) R V_\pi$$

Normalize (divide by $RC_1 C_2 L$) and factor out C_μ :

$$\left(s^3 + s \frac{(C_1 + C_2)}{C_1 C_2 L} + s^2 \frac{1}{RC_1} + \frac{1}{RC_1 C_2 L} \right) V_f = \frac{(s - \frac{g_m}{C_\mu}) R C_\mu}{RC_1 C_2 L} V_\pi$$

The loop-gain transfer function:

$$\frac{V_f}{V_\pi} = A(s) = \frac{\frac{RC_\mu}{RC_1 C_2 L} (s - \frac{g_m}{C_\mu})}{s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{RC_1 C_2 L}} = \frac{K N(s)}{D(s)}$$

Closed Loop Analysis - cont.

The closed loop equation (note the [positive feedback](#)):

$$T(s) = \frac{A(s)}{1 - A(s)} = \frac{K N(s)}{D(s) - K N(s)} \quad A(s) = \frac{\frac{RC_\mu}{RC_1 C_2 L} (s - \frac{g_m}{C_\mu})}{s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{RC_1 C_2 L}} = \frac{K N(s)}{D(s)}$$

where:

$$A(s) = \frac{K N(s)}{D(s)} \quad K = \frac{RC_\mu}{RC_1 C_2 L} \quad N(s) = s - \frac{g_m}{C_\mu} \approx -\frac{g_m}{C_\mu}$$

$$D(s) = s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{RC_1 C_2 L}$$

then:

$$D(s) - K N(s) = D(s) - \frac{-g_m R}{RC_1 C_2 L} = s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1 + g_m R}{RC_1 C_2 L}$$


Closed Loop Analysis - cont.

We know that the open loop system $A(s)$ is stable. It has poles in the left-half s -plane, since it is a passive RLC circuit. We also know that it has 3 stable poles. One is negative-real, the other 2 can be negative-real or LHP complex conjugates.

$$D(s) = s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{RC_1 C_2 L}$$

So, let's do a rough sketch of the root locus for a feedback system with a 3 stable pole $A(s)$.

Root Locus Characteristic

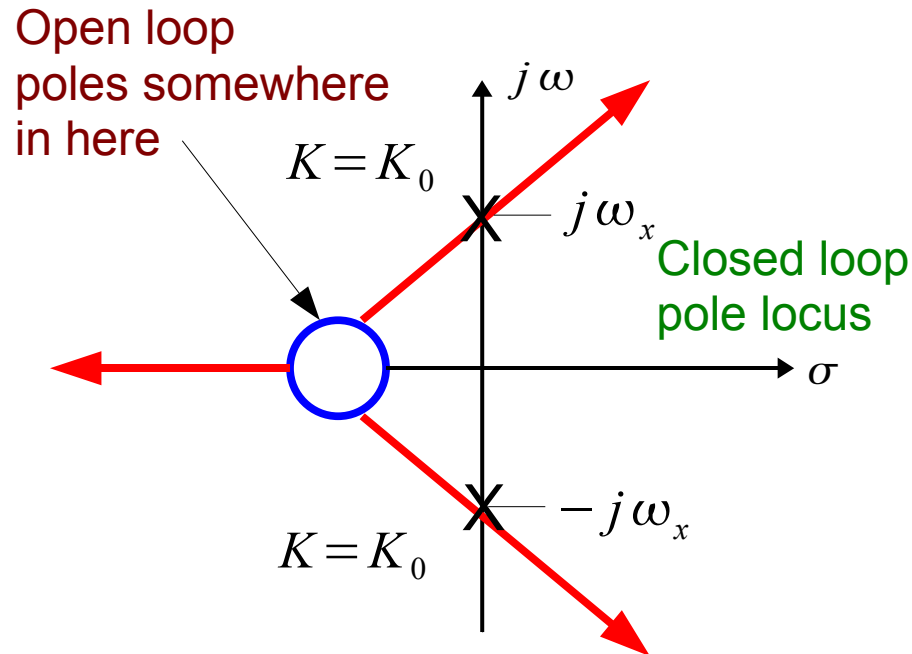

The loop will become unstable for any value of $K > K_0$.

Rather than sketch the root locus in more exacting detail – it has served its purpose by verifying that oscillation is possible.

Let's solve for the required K_0 .

Stability Limit Calculation

If the closed-loop system is at the stability limit point:

$$D(s) = (s+a)(s^2 + \omega_x^2)$$

Multiplying terms:

$$D(s) = s^3 + a s^2 + \omega_x^2 s + a \omega_x^2 \Rightarrow D(j\omega) = (a \omega_x^2 - a \omega^2) = j(\omega_x \omega - \omega^3)$$

to oscillate = 0

Match term by term with:

$$D(s) + K N(s) = s^3 + s^2 \frac{a}{RC_1} + s \frac{\omega_x^2 (C_1 + C_2)}{C_1 C_2 L} + \frac{a \omega_x^2 (1 + g_m R)}{RC_1 C_2 L}$$

$$a = \frac{1}{RC_1} \quad \omega_x^2 = \frac{1}{\left(\frac{C_1 C_2}{C_1 + C_2}\right) L} \quad a \omega_x^2 = \frac{1 + g_m R}{RC_1 C_2 L}$$

Stability Limit

$$a = \frac{1}{RC_1}$$

$$\omega_x^2 = \frac{1}{\left(\frac{C_1 C_2}{C_1 + C_2}\right)L} = \frac{C_1 + C_2}{C_1 C_2 L}$$

$$a \omega_x^2 = \frac{1 + g_m R}{RC_1 C_2 L}$$

To find the “gain” requirement for oscillation, equate:

$$\frac{1}{RC_1} \frac{C_1 + C_2}{C_1 C_2 L} = \frac{C_1 + C_2}{RC_1^2 C_2 L} = \frac{1 + g_m R}{RC_1 C_2 L} \Rightarrow 1 + g_m R = \frac{C_1 + C_2}{C_1}$$

a ω_x^2 $a \omega_x^2$

$$g_m R = \frac{C_1 + C_2 - C_1}{C_1} = \frac{C_2}{C_1}$$

Oscillator Design Summary

The oscillation frequency:

$$\omega_x = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}$$

The required feedback gain C_2/C_1 :

$$g_m R = \frac{C_2}{C_1}$$


To insure the start-up of oscillation:

$$g_m R > \frac{C_2}{C_1}$$

Comments:

1. Unfortunately we don't control "R".
2. We can fix g_m and adjust C_2/C_1 and adjust "L" to keep ω_x constant.
2. We can adjust g_m through the bias current I_C and set C_2 and C_1 at convenient values, say $C_2 = C_1 = C$. We can now choose L .

Practical Colpitts Oscillator Circuit

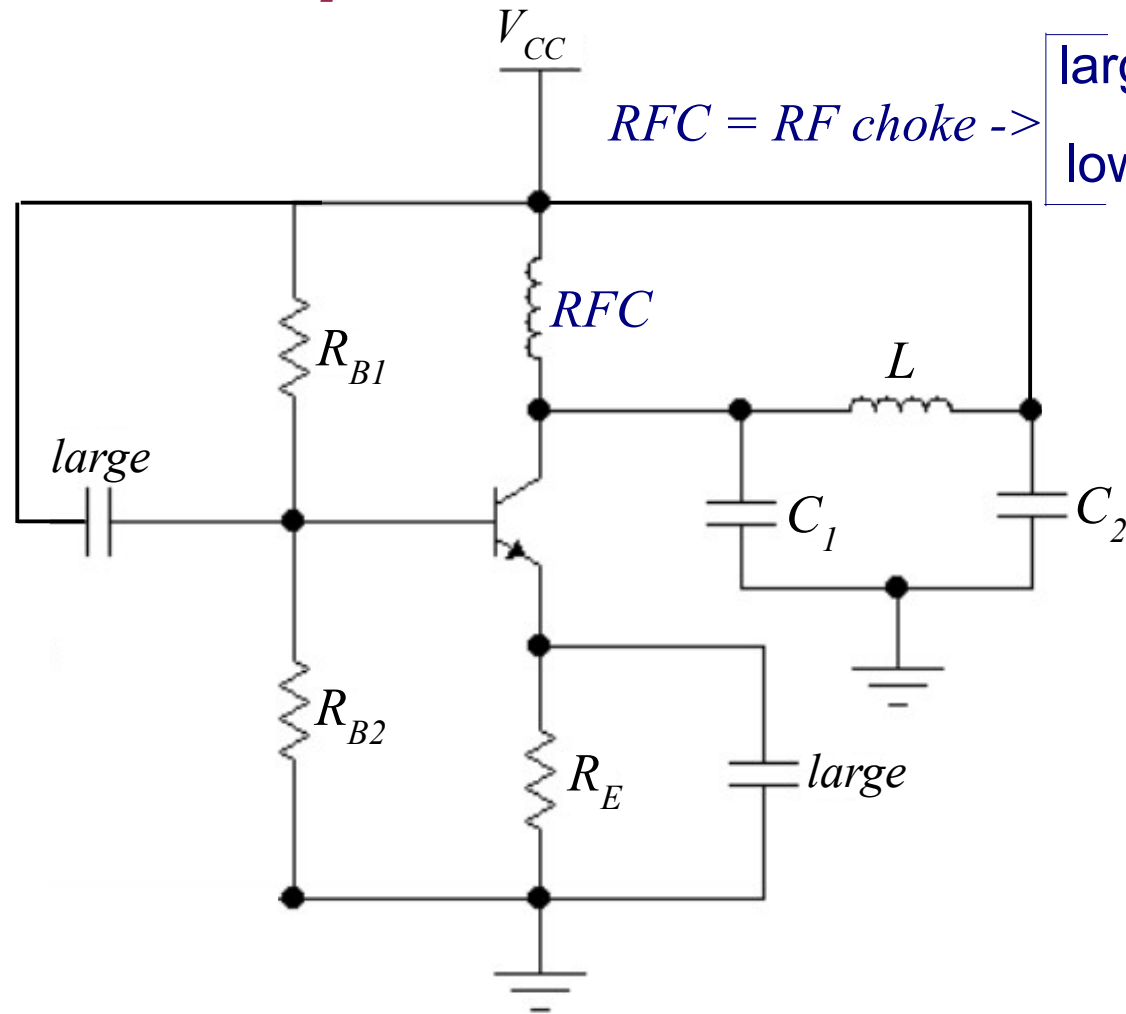

$RFC = RF\ choke \rightarrow$ large reactance at ω_0
low resistance at dc