

References

Link Power Electronics reference article

Link Good Synquor example

Constants

- $P_O := 200W$ Load power
- $V_{I_max} := 36V$ Maximum input voltage
- $V_{I_min} := 18V$ Minimum input voltage
- $\eta := 83\%$ Load power converter conversion efficiency

Analysis

Switching Supply Input Resistance is Negative (at least for low frequencies)

$$P_I = \frac{P_O}{\eta} = V_I \cdot I_I$$

Definition of power and efficiency

$$I_I := \frac{P_O}{\eta \cdot V_{I_max}} = 6.69A$$

Substitute example values, this would be the input current.

Definition of differential input resistance

$$r_d(P, I_I) := \frac{d}{dI_I} \frac{P}{I_I} \rightarrow -\frac{P}{I_I^2}$$

$$r_d(V_I, I_I) := r_d(V_I \cdot I_I, I_I) \rightarrow -\frac{V_I}{I_I}$$

$$r_d(V_{I_max}, I_I) = -5.38\Omega$$

Example differential resistance SynQuor example of actual input resistance

Switching Supply is Equivalent to a DC Transformer

Ignoring the inefficiency

$$V_I \cdot I_I = V_O \cdot I_O$$

$$\frac{V_I}{V_O} = \frac{I_O}{I_I} = n$$

n being equivalent to the turns ratio. n = D where n is the duty cycle of the switcher

Let $R_L = V_O/I_O$

$$V_I = V_O \cdot n = \frac{V_O}{I_O} \cdot n \cdot I_O = n \cdot R_L \cdot I_O \Rightarrow I_I = \frac{I_O}{n}$$

$$r_d(n, R_L) := r_d\left(n \cdot R_L \cdot I_O, \frac{I_O}{n}\right) \rightarrow -R_L \cdot n^2$$

Very similar to the impedance transformation formula for a transformer.

Analysis of Typical Example

Example of a Typical Zero-Current Switcher (ZCS).



Remember that this note was by a Vicor PLM person.

Fig. 1. A commercial dc-dc converter that employs zero current switching.

Rule of thumb is that the source impedance should be less than 10% that of the supply input impedance.

$$Z_{S_max} := \left| \frac{V_{LL}}{P_{LL}} \cdot V_{LL} \cdot \frac{1}{10} \right|$$

V_{LL} is the low line input voltage
 P_{LL} is the low line input power of the module

Uncompensated Case

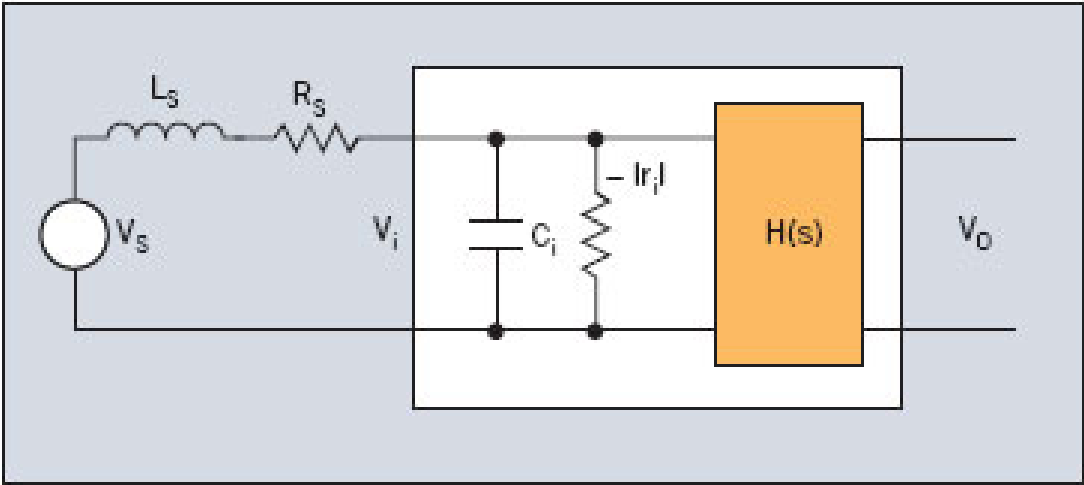


Fig. 2. A typical dc-dc converter connects to a power source having its own internal impedance, which is not zero.

eq1 := $H(s) \cdot V_S \cdot \frac{\frac{1}{s \cdot C_i} \cdot -r_i}{\frac{1}{s \cdot C_i} + -r_i}$ simplify \rightarrow

$R_S + s \cdot L_S + \frac{1}{\frac{1}{s \cdot C_i} + -r_i}$

The denominator is referred to as the characteristic polynomial and determines the stability of the system.

eq2 := $\frac{\text{denom}(\text{eq1})}{r_i}$ simplify \rightarrow

This is the characteristic polynomial of this equation.

To ensure negative roots, all coefficients must be positive (Decartes' rule of sign)

eq3 := eq2 coeffs, s \rightarrow

eq3₀ > 0 $\rightarrow 1 - \frac{R_S}{r_i} > 0$ (1) $r_i > R_S$ ✓ Same result as in the article

- - - L_S ✓ Same result as in the article

Compensated Power Supply Input

eq3₁ > 0 → C_i · R_S − $\frac{1}{r_i}$ > 0 (2) $R_S > \frac{1}{C_i \cdot r_i}$ ✓

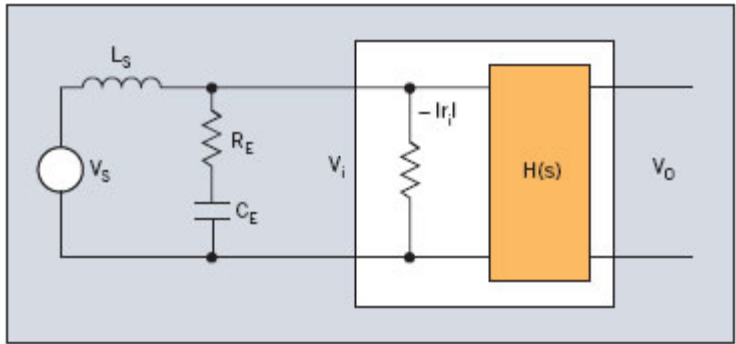


Fig. 3. A common practice is to put a large capacitor in parallel with the input stage of a dc-dc converter.

Compared to Figure 2, the resistance, R_S, has been removed to simplify the analysis.

eq4 := $H(s) \cdot \frac{\frac{1}{\frac{1}{s \cdot C_E} + R_E} \cdot \frac{1}{r_i}}{s \cdot L_S + \frac{1}{\frac{1}{s \cdot C_E} + R_E} - \frac{1}{r_i}}$ simplify →

eq5 := denom(eq4) →

To ensure negative roots, all coefficients must be positive

eq7 := eq6₁ > 0 →

eq8 := eq6₂ > 0 →

(3) $r_i > \frac{L_S}{C_E \cdot R_E}$
(4) $r_i > R_E$

✓ Same result as in the Power Electronics and Synquor articles.
✓ Same result as in the Power Electronics and Synquor articles.

$r_i > R_E > \frac{L_S}{C_S \cdot r_i}$

Eq. 4 states that R_E should be smaller than r_i. However, from Eq. 3, it is clear that if R_E is made too small, oscillation will result. This means that adding low-ESR capacitance may not resolve a stability problem – more loss is needed.

From Eq. 3, it is also possible to see that a bigger input inductance requires a larger input capacitance to compensate its effects. Also, lower input differential resistance, r_i, means a larger input capacitance is needed to ensure stable operation. Once the value of the input inductor, L_S, and input incremental resistance, r_i, are known, it is possible to replace the numbers in Eq. 3 and 4 to find the optimal combination for C_E with the proper ESR.

Appendix

Example of an Actual Power Supply Input Impedance

Figure 2 shows $|Z_I|$ versus frequency for SynQor's 48V_{IN}, 3.3V_{OUT}, 30A dc/dc converter. As can be seen, at low frequencies $|Z_I|$ is resistive (actually, we need to look at the phase of Z_I , which is -180° at low frequencies, to see that it is negative). Around 1 kHz the magnitude starts to roll off with a slope of -20dB per decade. We can model this as a capacitor C in parallel with R_N . Similarly, a more complex circuit can model the resonant dynamics that show up around 20 kHz in the plot of $|R_N|$. For this discussion, however, we will just use the simple $R_N C$ model.

